



DCC Decoder Tester

Version 2

Before fitting a new DCC decoder into one of your locomotives, it makes sense to check that it is operational. This can be done with a simple Decoder Tester, shown in the schematic overleaf, which is constructed from a set of resistors and light-emitting diodes. Any colour or type of LEDs can be used, and all resistors, with the exception of R1 are 0.5 watt rated. R1 should have a 2 watt rating as a minimum (and preferably 3 watt), since it is intended to provide a load which stands in for the locomotive motor during programming, and will have to withstand the full DCC track voltage – nominally 14 volts for HO-scale.

Connections to the track and the decoder can be made using flying leads from the Tester, terminated in miniature crocodile clips (preferably insulated to avoid inadvertent short circuits), and which are plugged on to sets of pin headers, as can be seen in the photographs of a sample Decoder Tester shown later in the document. Alternatively, you can make up wiring harnesses with appropriate sockets to take the NMRA plugs fitted to some decoders, or you can fit sets of spring or screw terminals, again as shown in the photographs. The 4-position spring terminal blocks used in the example Tester (insert small instrument screwdriver to open each contact) are made by Camden – part number CSTBV23/4.

To use the Decoder Tester, connect to the decoder first, then attach the final two input leads to the track, or direct to the programming outputs from your DCC Command Station. If all is well, both LEDs L1a and L1b should light when power is applied to the track by the Command Station. If only one of these LEDs is lit then it indicates that plain DC is being applied to the Tester instead of DCC power (14 volts AC).

The other LEDs are driven from the outputs of the decoder under test. New decoders come with their address set to the default value of 03, so send DCC commands to this address and check that the appropriate LEDs light –

L2a = Motor Forward

L5 = Function 1

L2b = Motor Reverse

L6 = Function 2

L3 = Forward Light


L7 = Function 3 (if present)

L4 = Reverse Light



L8 = Function 4 (if present)

L9 = Function 5 (if present)

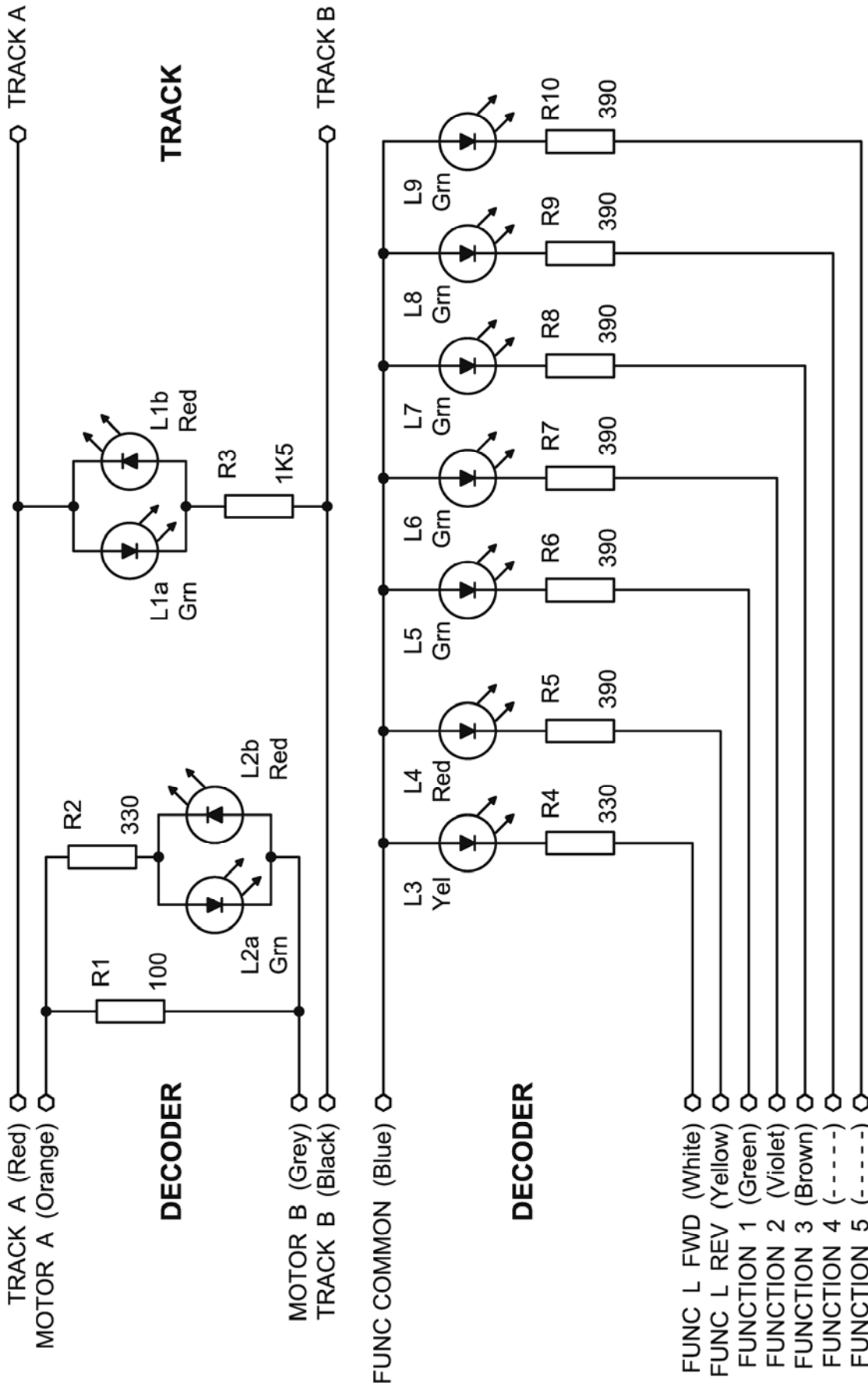A suggested layout for constructing the tester on stripboard is shown on the page after the schematic, and this is followed by a set of photographs showing a built tester and its various connecting harnesses.



A-Track Decoder Tester

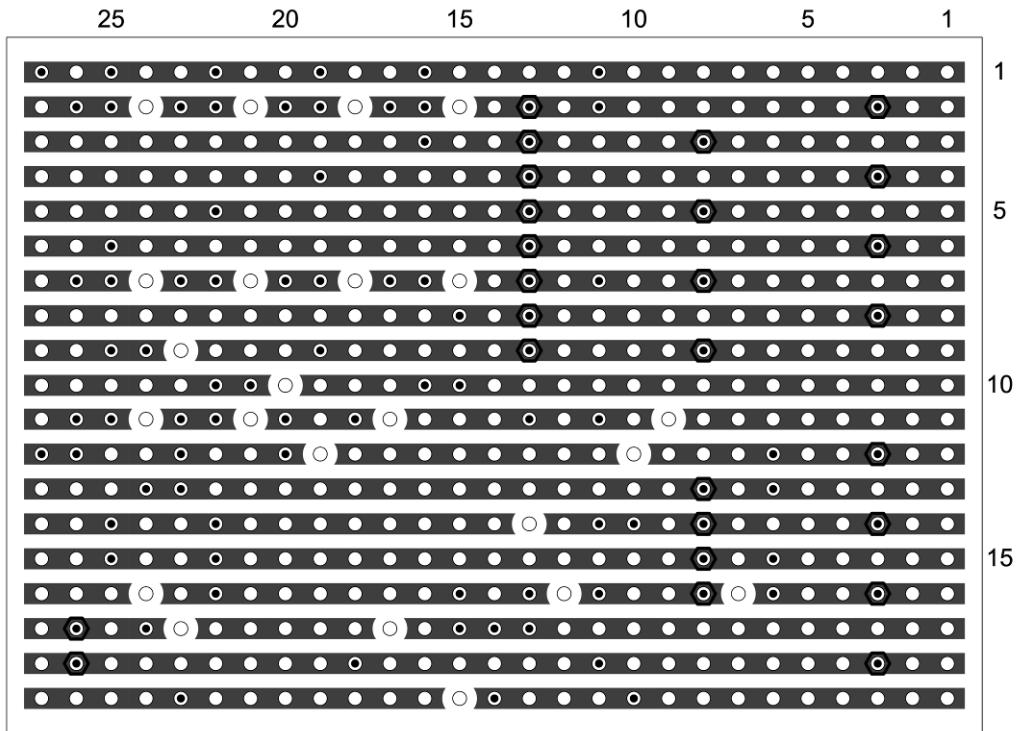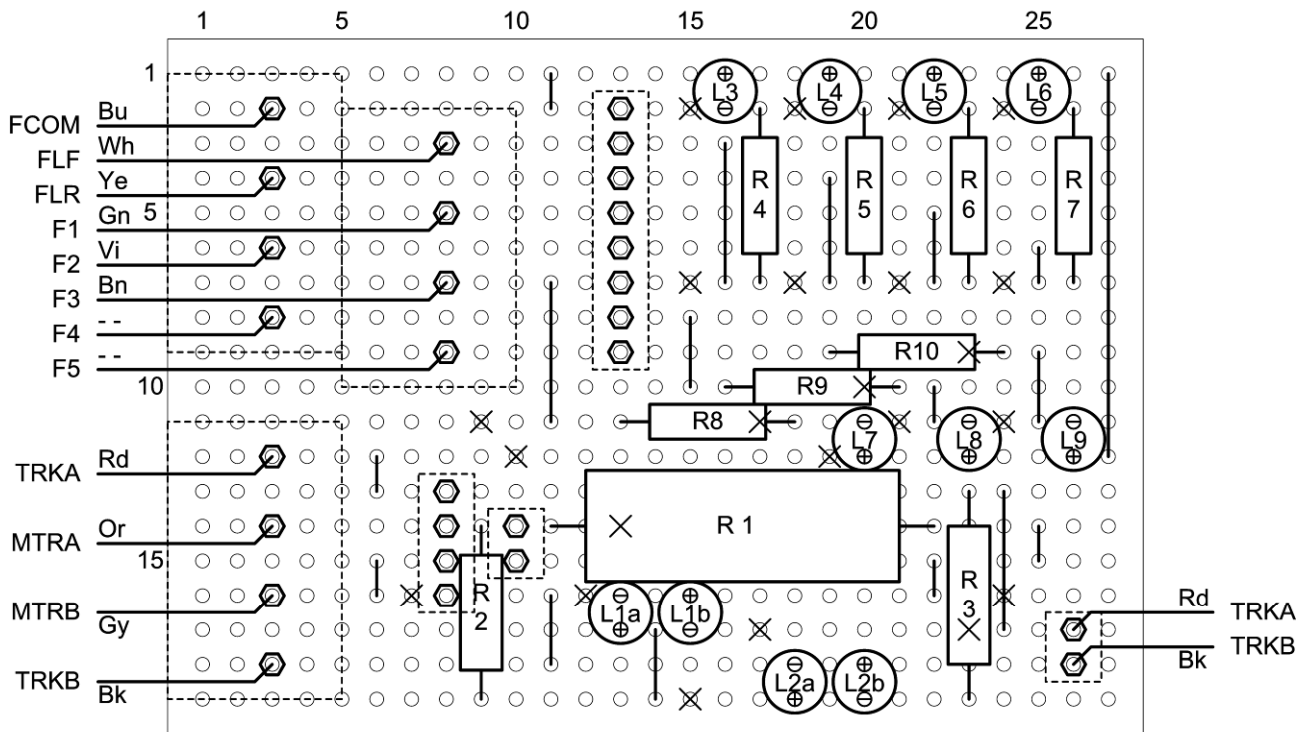

A-Train Decoder Tester

DCC_TESTER_BOARD_2.VSD

Stripboard Layout

Copyright © JT Chamberlain 1999 - 2013 All rights reserved

